

# Analogue to Digital Conversion

---

- Turns electrical input (voltage/current) into numeric value
- Parameters and requirements

## Resolution

the granularity of the digital values

## Integral Non-Linearity

proportionality of output to input

## Differential Non-Linearity

uniformity of digitisation increments

## Conversion time

how much time to convert signal to digital value

## Count-rate performance

how quickly a new conversion can begin after a previous event

## Stability

how much values change with time

# Resolution


- To convert an analogue value, eg voltage, to digital two parameters are required  
range and number of bits

$$\text{quantum} = V = (V_{\max} - V_{\min}) * 2^{-N} \quad \text{referred to as 1LSB (least significant bit)}$$

- eg 10 bits =  $2^{10} = 1024$ ,  $V_{\max} - V_{\min} = 1V \Rightarrow V = 1V/1024 \quad 1mV$

- Ideal ADC behaviour

probability vs amplitude

 


- Real ADC behaviour

noise in digitisation process

smears resolution

$$\text{noise} < V/4$$

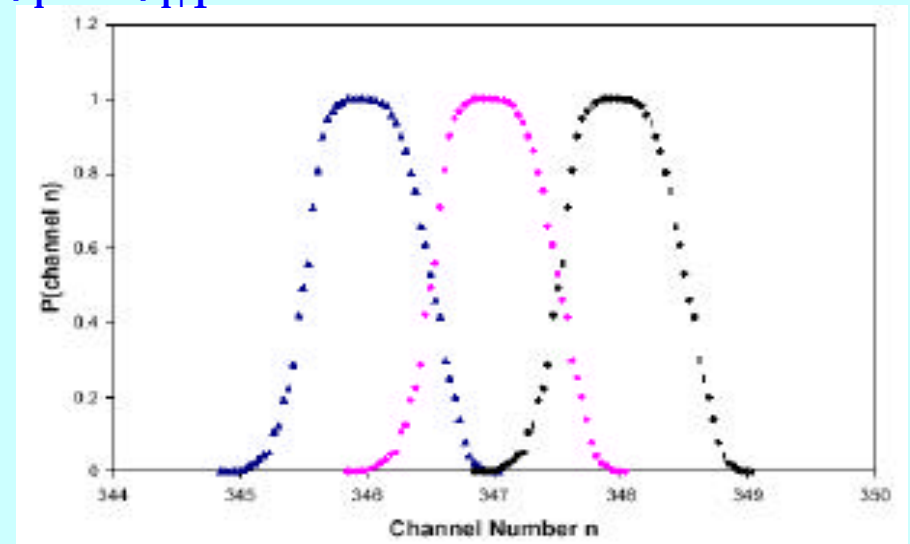

# Speed vs resolution

•from Analog Devices ADC selection guide

bits per sec (or samples per sec)

		Throughput rate (bps)					
		<10k	10-100k	100k-1M	1-10M	10-100M	>100M
Resolution (bits)	17		-----	-----	-----	-----	-----
	14-16						-----
	12-13	-----					
	10-11	-----					
	8-9	-----	-----				
	8	-----	-----	-----	-----		-----

Maximum speed 200Mbps 12 bits 1.3W single channel

210Mbps 10bits 2.4W single channel

Maximum resolution 24 bits 6.4kbps

•What determines this relationship?

# Integral non-linearity



- Output value  $D$  should be linearly proportional to  $V$

check with plot

for more precise evaluation of INL

fit to line and plot deviations

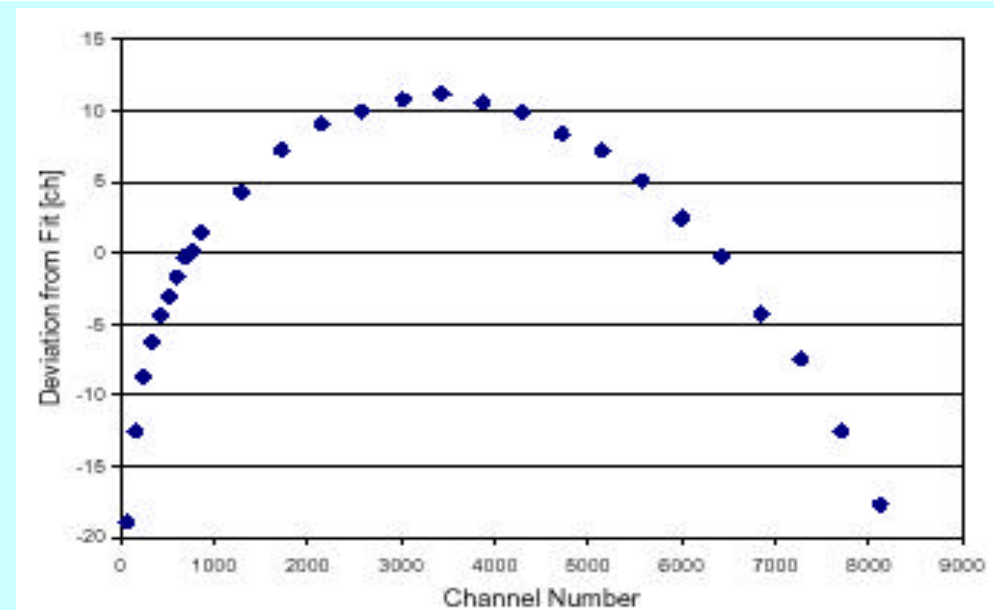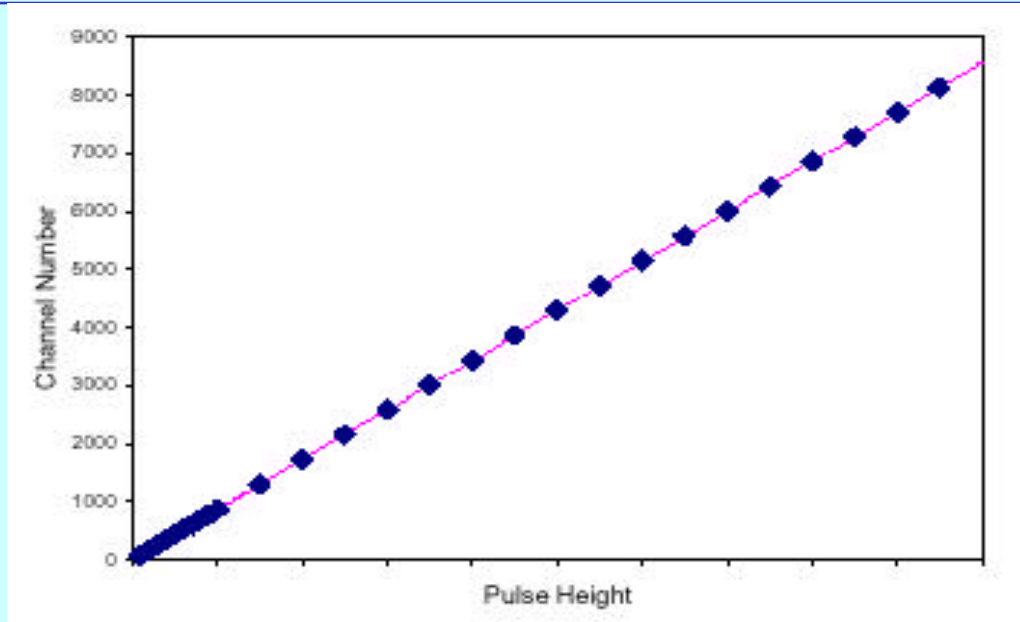plot  $D_i - D_{\text{fit}}$  vs  $n_{\text{chan}}$



# Differential non-linearity

- measures non-uniformity in channel profiles over range

$$\text{DNL} = V_i / \langle V \rangle - 1$$


$V_i$  = width of channel  $i$

$\langle V \rangle$  = average width

- rms or worst case values may be quoted

DNL  $\sim$  1% typical but  $10^{-3}$  can be achieved

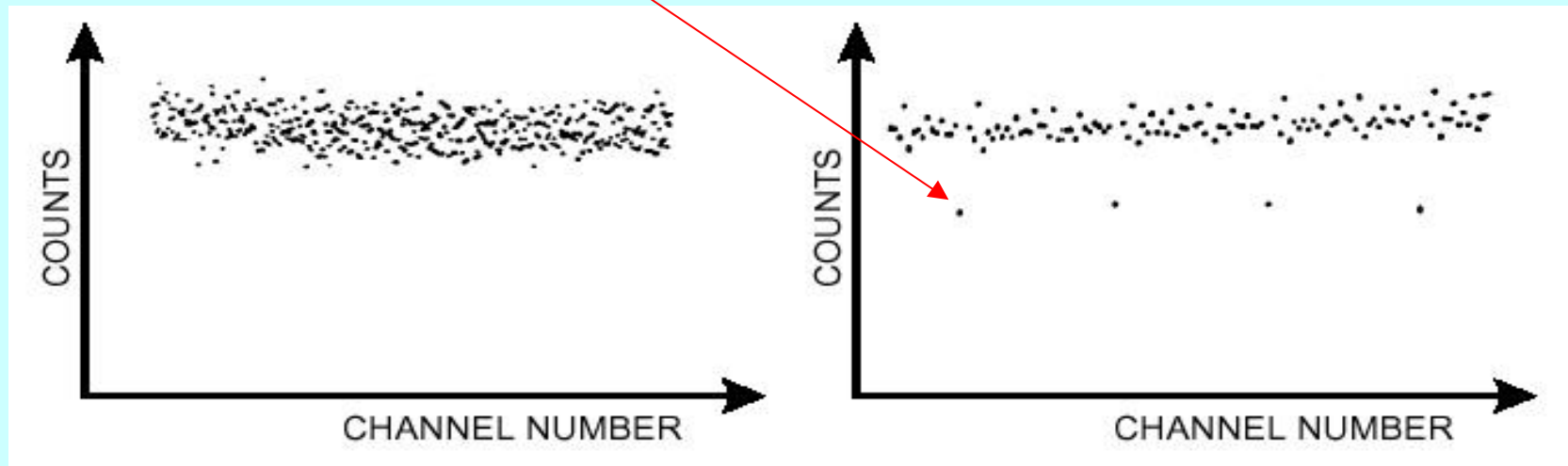can show up systematic effects, as well as random



# Other variables

---

- **Conversion time**

  - finite time is required for conversion and storage of values

  - may depend on signal amplitude

  - gives rise to dead time in system

    - ie system cannot handle another event during dead time

    - may need accounting for, or risk bias in results*

- **Rate effects**

  - results may depend on rate of arrival of signals

  - typically lead to spectral broadening

- **Stability**

  - temperature effects are a typical cause of variations

- **A partial solution to most of these problems is regular calibration, preferably under real operating conditions, as well as control of variables**

# Parallel (Flash) ADC

- Input value is compared simultaneously...

- against a set of comparators

$2^N$  comparators required for N bits

Threshold values defined by

resistor chain

relative accuracy important,

not absolute values

- Pros

short conversion time

*eg 10bits @ 40MHz*


- Cons

limited resolution,

*size of IC grows with N*

DNL ~ 1%

power consumption

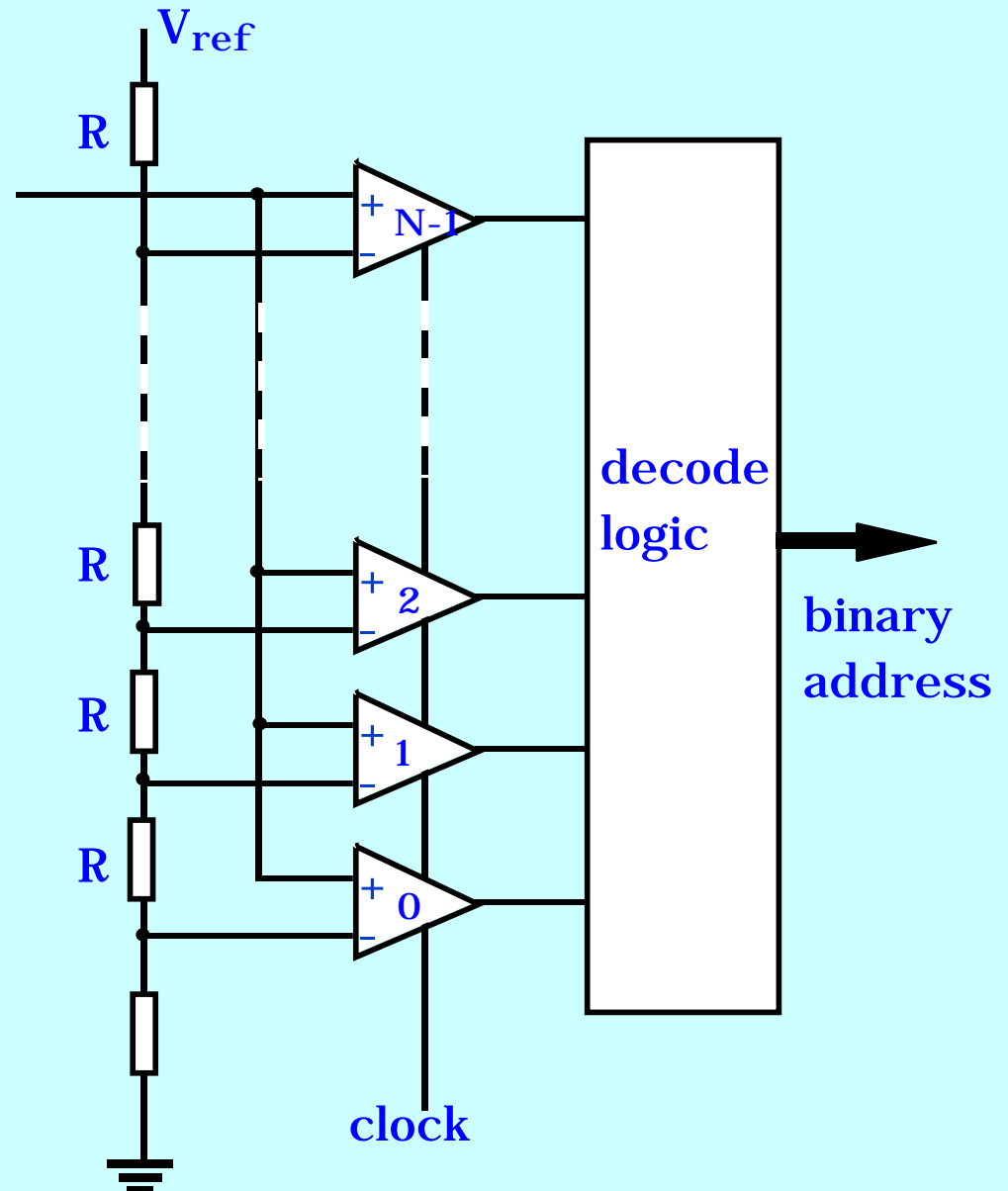

# Successive approximation ADC

- analogous to binary search


generate  $V_{ref} = V \times (2^{N-1}, 2^{N-2}, \dots 2^0)$  in N steps

set bit = 1

if  $V_{in} > V_{ref}$

leave

else bit = 0

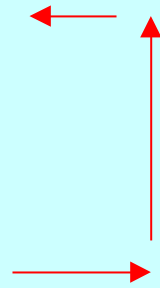

- Pros


speed ~  $\mu$ sec

high resolution

- Cons

DNL 10-20%

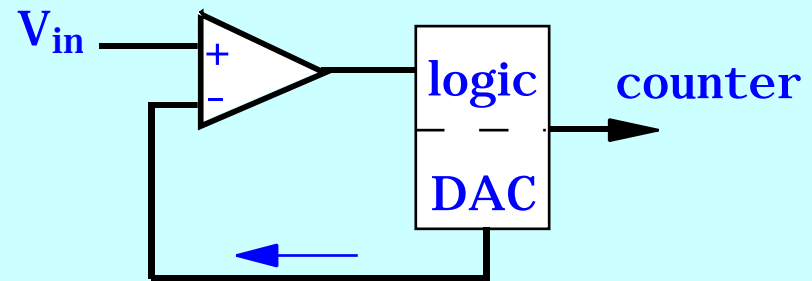*very precise resistors required with DAC for  $V_{ref}$*



DAC = digital to  
analogue converter  
ie number -> voltage



# Single slope (Wilkinson) ADC

- **Single slope conversion**

input signal charges capacitor  
discharged by constant current  
counter (eg 200MHz) times discharge


- **Pros**

Excellent DNL

- **Cons**

modest absolute accuracy  
slow, and conversion time depends  
on amplitude
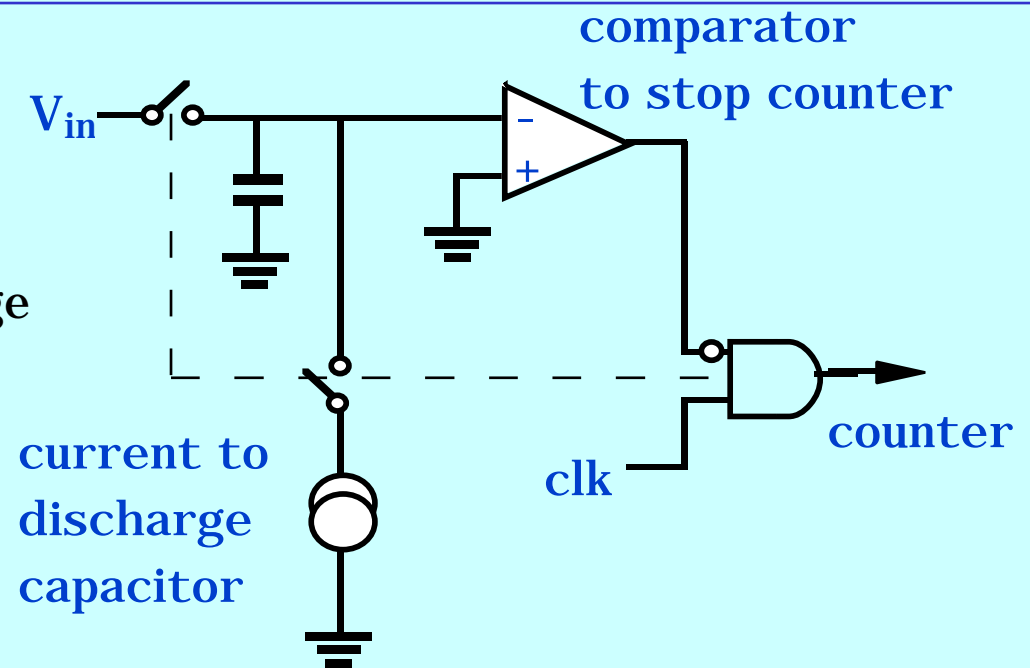
$$T_{\text{conv}} = nT \quad \text{eg } T = 10\text{ns, } 13 \text{ bits} \quad T_{\text{conv}} = 82\mu\text{s}$$



- **Dual slope conversion reduces systematic (absolute) errors**

charge C with constant current and then measure time for discharge

charge and discharge subject to same comparator and capacitor variations

# Time to Digital Conversion (TDCs)

---

- Count clock pulses between start and stop pulses

up to ~1GHz, limited by technology so  $t \approx 1\text{ns}$

capable of digitising more than one hit in an acquisition

*provided logic is sufficient*

- Analogue ramp

for greater precision,  $t \approx 10\text{ps}$

charge capacitor with constant current source

start pulse: turns on current

stop pulse: turns off

then measure  $V$  on storage capacitor using ADC

*can't accept more than one signal in digitising period*